

# ASSIGNMENT

Morri Bharath

20211a04e1@bvrit.ac.in

IITH - Future Wireless Communications (FWC)

## CONTENTS


- 1 Question
- 2 Components
- 3 Truth Table
- 4 Logical Diagram
- 5 Implementation

## 3 TRUTH TABLE

|   |          |          |          |          |
|---|----------|----------|----------|----------|
|   | <b>a</b> | <b>b</b> | <b>c</b> | <b>z</b> |
| 2 | 0        | 0        | 0        | 0        |
|   | 0        | 0        | 1        | 1        |
| 2 | 0        | 1        | 0        | 0        |
|   | 0        | 1        | 1        | 0        |
| 2 | 1        | 0        | 0        | 1        |
|   | 1        | 0        | 1        | 1        |
| 2 | 1        | 1        | 0        | 1        |
|   | 1        | 1        | 1        | 1        |

Truth table Boolean Function "z"

## 1 QUESTION

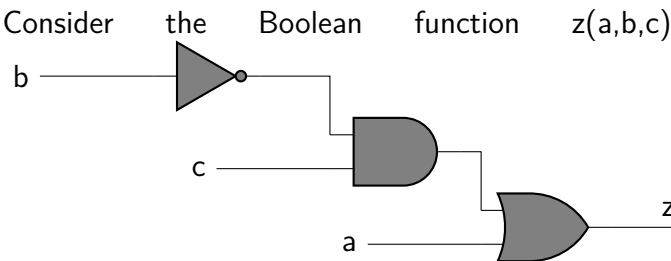


- 1)  $z = \sum(0, 1, 3, 7)$
- 2)  $z = \sum(1, 4, 5, 6, 7)$
- 3)  $z = \sum(2, 4, 5, 6, 7)$
- 4)  $z = \sum(2, 3, 5)$

## 2 COMPONENTS

| Component   | Values  | Quantity |
|-------------|---------|----------|
| Arduino     | UNO     | 1        |
| JumperWires | M-M     | 6        |
| Breadboard  |         | 1        |
| LED         |         | 1        |
| Resistor    | 220ohms | 1        |

Figure.a

## 4 LOGICAL DIAGRAM

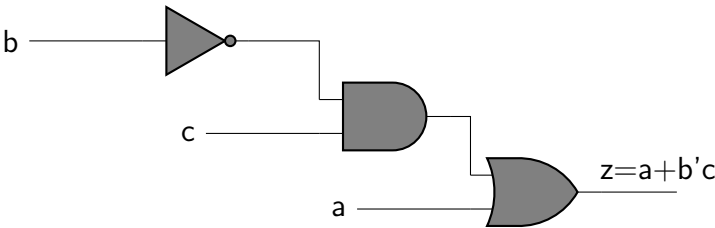

## 5 IMPLEMENTATION

| Arduino PIN | INPUT | OUTPUT |
|-------------|-------|--------|
| 2           | a     |        |
| 3           | b     |        |
| 4           | c     |        |
| 5           |       | z      |

Connections

### a) Procedure

- 1. Connect the circuit as per the above table.
- 2. Connect the one end of the resistor to anode of LED and cathode of LED to ground.
- 3. Connect the output pin to another end of resistor.
- 4. Connect inputs to Vcc for logic 1, ground for logic 0.

5. Execute the circuit using the below code.

**<https://github.com/BharathMorri/cs282020/blob/main/asg.cpp>**

6. Change the values of a,b,c in the code and verify the Truth Table.