

ASSIGNMENT

Morri Bharath

20211a04e1@bvr.it.ac.in

IITH - Future Wireless Communications (FWC)

CONTENTS


- 1 Question
- 2 Components
- 3 Truth Table
- 4 Logical Diagram
- 5 Implementation

3 TRUTH TABLE

| | a | b | c | z |
|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 0 |
| | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| | 1 | 1 | 1 | 1 |

Truth table Boolean Function "z"

1 QUESTION

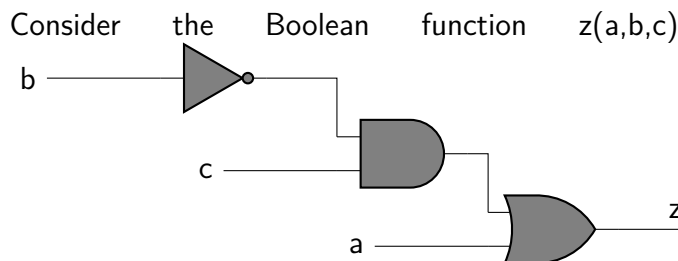

Which of the following minterm lists represents the circuit given above?

- 1) $z = \sum(0, 1, 3, 7)$
- 2) $z = \sum(1, 4, 5, 6, 7)$
- 3) $z = \sum(2, 4, 5, 6, 7)$
- 4) $z = \sum(2, 3, 5)$

2 COMPONENTS

| Component | Values | Quantity |
|-------------|---------|----------|
| Arduino | UNO | 1 |
| JumperWires | M-M | 6 |
| Breadboard | | 1 |
| LED | | 1 |
| Resistor | 220ohms | 1 |

Figure.a

4 LOGICAL DIAGRAM

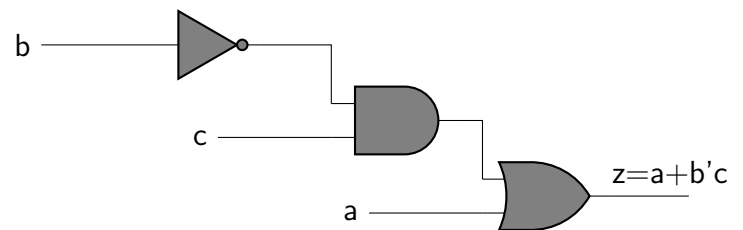


Fig. 1

5 IMPLEMENTATION

| Arduino PIN | INPUT | OUTPUT |
|-------------|-------|--------|
| 2 | a | |
| 3 | b | |
| 4 | c | |
| 5 | | z |

Connections

a) Procedure

1. Connect the circuit as per the above table.
2. Connect the one end of the resistor to anode of LED and cathode of LED to ground.
3. Connect the output pin to another end of resistor.
4. Connect inputs to Vcc for logic 1, ground for logic 0.

5. Execute the circuit using the below code.

[https://github.com/BharathMorri
/cs282020/blob/main/asg.cpp](https://github.com/BharathMorri/cs282020/blob/main/asg.cpp)

6. Change the values of a,b,c in the code and verify the Truth Table.